

# HKN ECE 342 Final Worksheet - Cramming Carnival

---

## DC Analysis

### Transistor Parameters

MOSFETs:

$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2; V_{TN} = 1 \text{ V}$$


$$\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2; |V_{TP}| = 1 \text{ V}$$

BJTs:

$$\beta = 99; V_{BE, \text{on}} = 0.7 \text{ V}$$
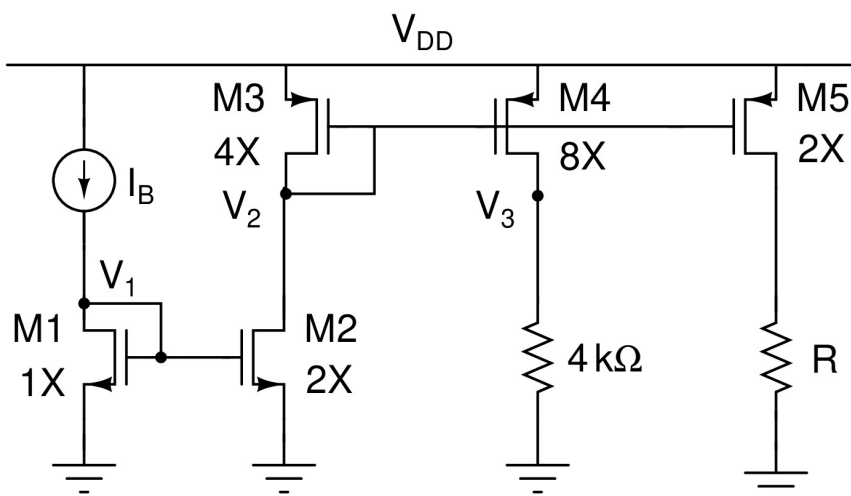
### Problem 1


For this problem, refer to the circuit below. Use  $V_{DD} = 5 \text{ V}$ ,  $I_B = 200 \mu\text{A}$ ,  $1X = \frac{100}{1}$ .



- (a) Determine the DC voltages  $V_1$ ,  $V_2$ , and  $V_3$ .
- (b) Determine the value of  $R$  such that  $M5$  is biased at the edge of saturation.
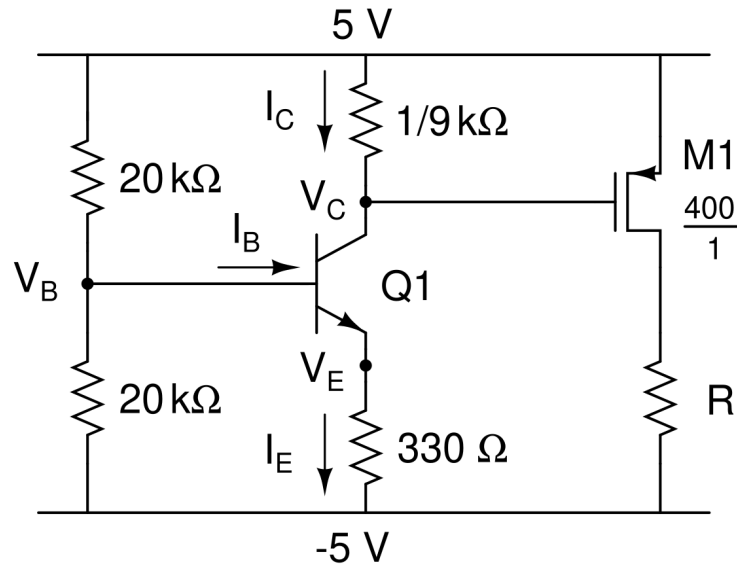
## Problem 2

For this problem, refer to the circuit below.




- Determine the DC currents and voltages  $V_B$ ,  $V_E$ ,  $V_C$ ,  $I_B$ ,  $I_E$ , and  $I_C$  of Q1. What is its region of operation?
- Determine the value of  $R$  such that M1 is biased at the edge of saturation.

## Small-Signal Analysis

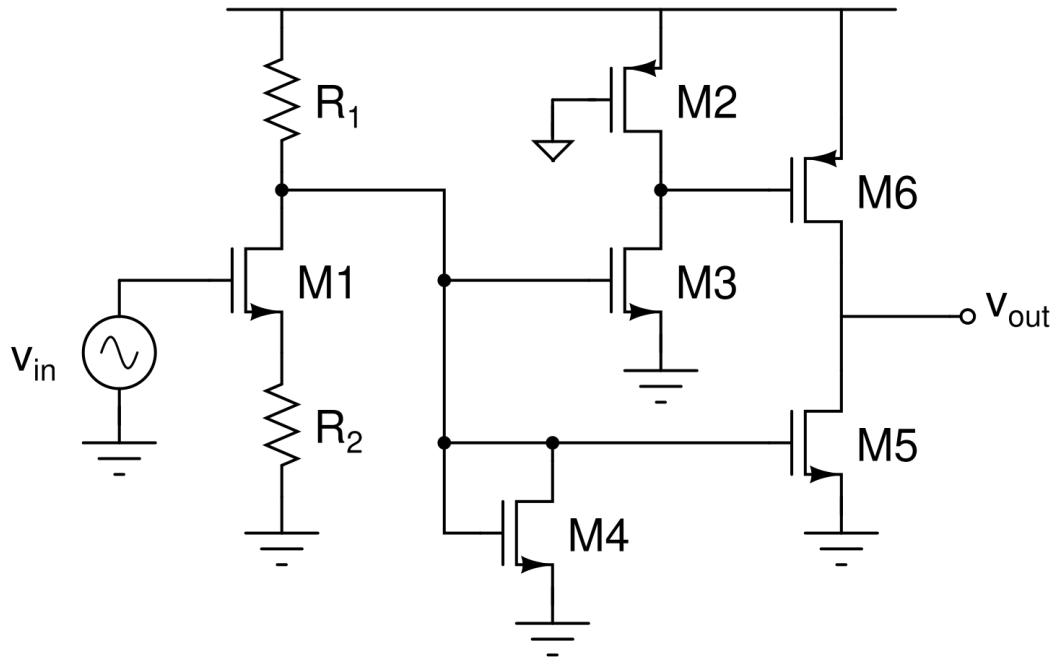
### Problem 1

Determine the values of  $G_M$ ,  $R_{OUT}$ , and  $A_v = v_{out}/v_{in}$  of this amplifier. Assume all MOSFETs are biased in saturation. Do not assume  $r_{ds} = \infty$ , though you can assume  $g_m r_{ds} \gg 1$ .



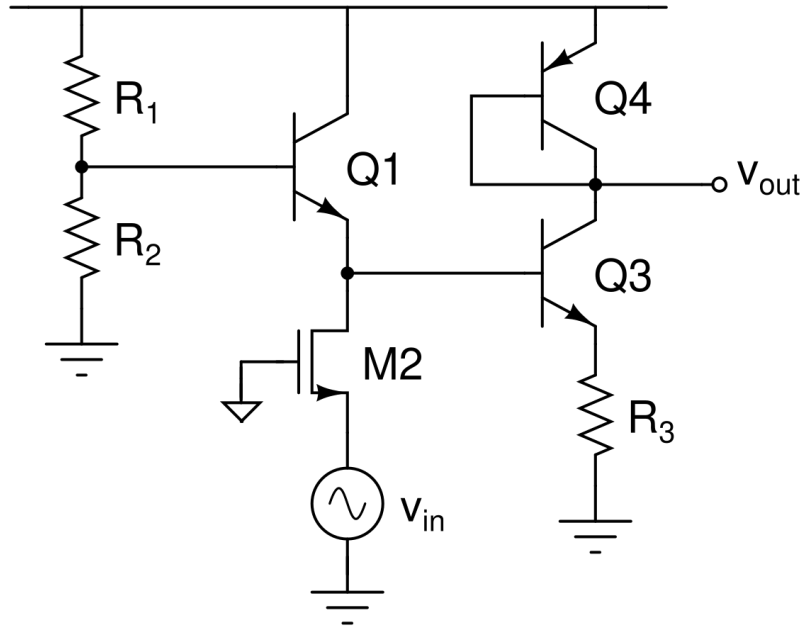
## Problem 2

Determine the values of  $G_M$ ,  $R_{OUT}$ , and  $A_v = v_{out}/v_{in}$  of this amplifier. Assume all MOSFETs are biased in saturation, all BJTs are biased in forward active mode,  $r_{ds} \neq \infty$ ,  $r_0 = \infty$ , and  $g_m r_{ds} \gg 1$ .



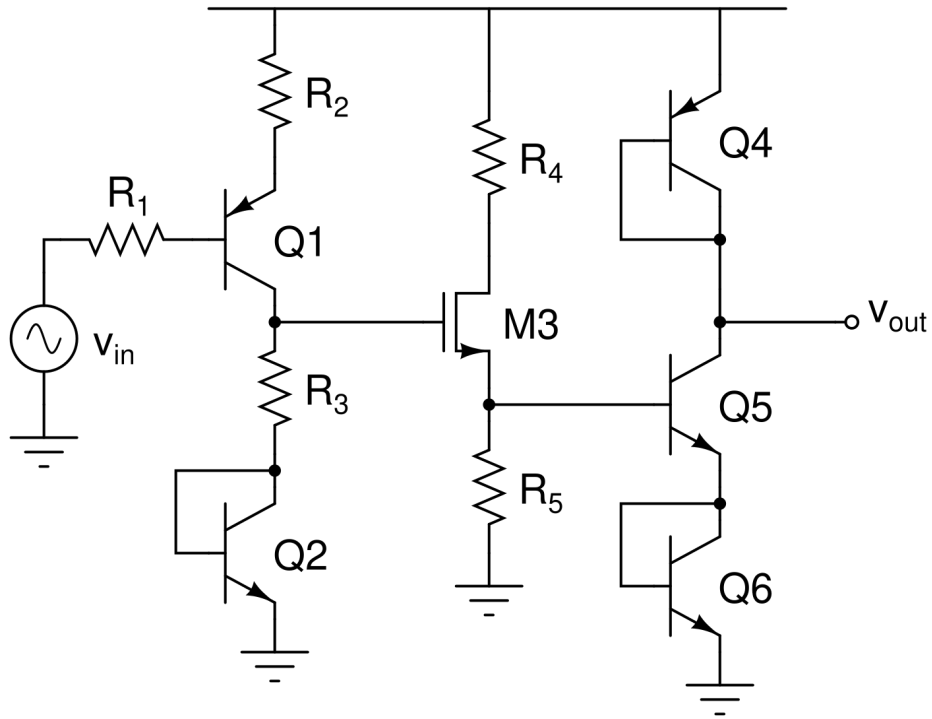
### Problem 3

Determine the values of  $G_M$ ,  $R_{OUT}$ , and  $A_v = v_{out}/v_{in}$  of this amplifier. Assume all MOSFETs are biased in saturation, all BJTs are biased in forward active mode,  $r_{ds} \neq \infty$ ,  $r_0 = \infty$ , and  $g_m r_{ds} \gg 1$ .



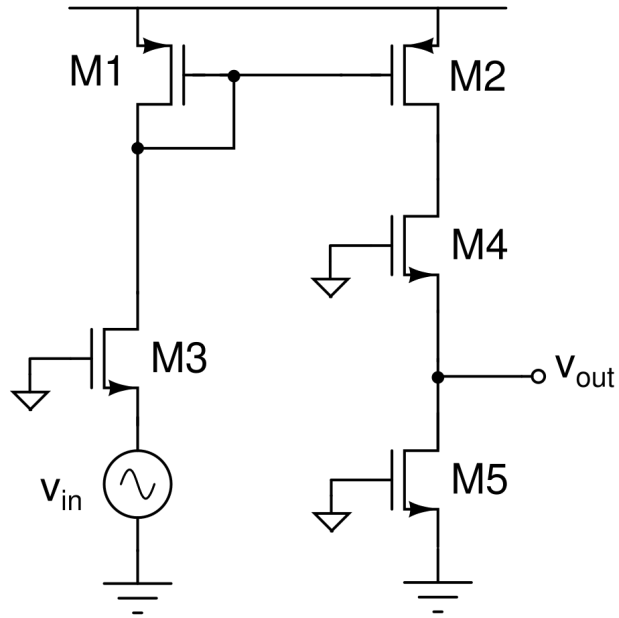
### Problem 4

Determine the values of  $G_M$ ,  $R_{OUT}$ , and  $A_v = v_{out}/v_{in}$  of this amplifier. Assume all MOSFETs are biased in saturation. Do not assume  $r_{ds} = \infty$ , though you can assume  $g_m r_{ds} \gg 1$ .


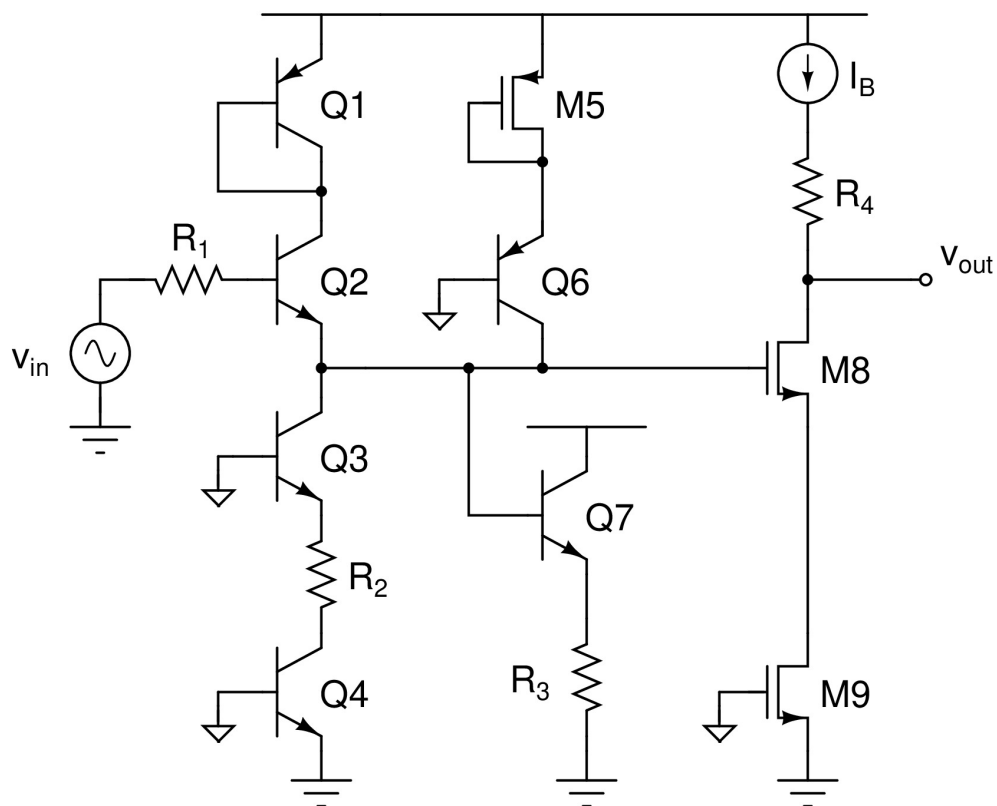
### Problem 5

Determine the values of  $G_M$ ,  $R_{OUT}$ , and  $A_v = v_{out}/v_{in}$  of this amplifier. Assume all MOSFETs are biased in saturation, all BJTs are biased in forward active mode,  $r_{ds} \neq \infty$ ,  $r_0 = \infty$ , and  $g_m r_{ds} \gg 1$ .



## Bode Plots

### Problem 1

For the following amplifier transfer functions, **(i)** plot the magnitude response, **(ii)** determine the unity gain frequency, and **(iii)** plot the phase response:

**(a)**

$$H(s) = \frac{10^4}{s(1 + s/10^3)}$$

**(b)**

$$H(s) = \frac{2000(1 + s/10^2)}{(1 + s/10)(1 + s/10^3)(1 + s/10^4)}$$

**(c)**

$$H(s) = \frac{4000(1 + s/10^2)}{(1 + s/10)(1 + s/10^4)^2}$$




## Problem 2

For each of the amplifier transfer functions in Problem 1, determine the incremental output voltage response  $v_{out}(t)$  to an incremental input voltage  $v_{in}(t) = 10 \cos(10^3 \cdot t)$  mV.

## Open Circuit Time Constants

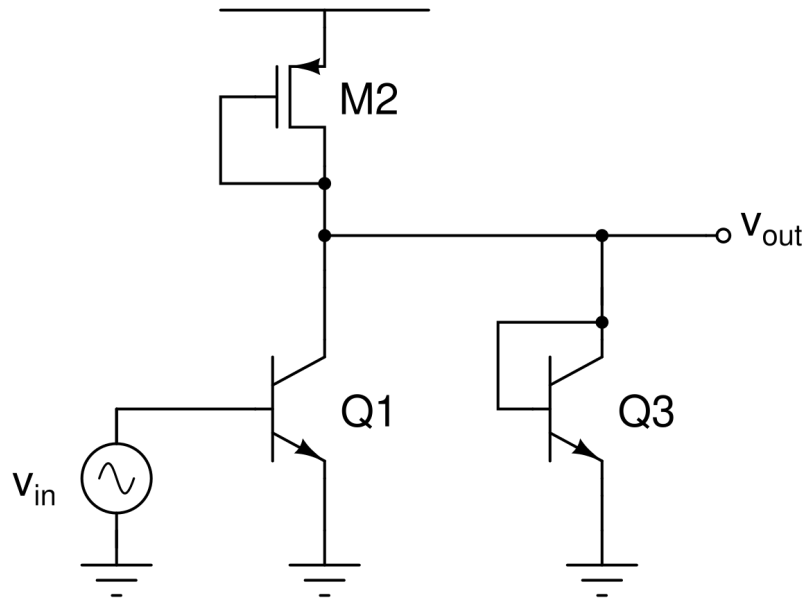
### Problem 1

Use the open-circuit time constant method to estimate the -3 dB frequency,  $\omega_{-3\text{dB}}$ , of this amplifier. Consider  $C_{gs}$ ,  $C_{gd}$ ,  $C_{\pi}$ ,  $C_{\mu}$ , and  $r_{ds}$ . Ignore  $r_o$ .



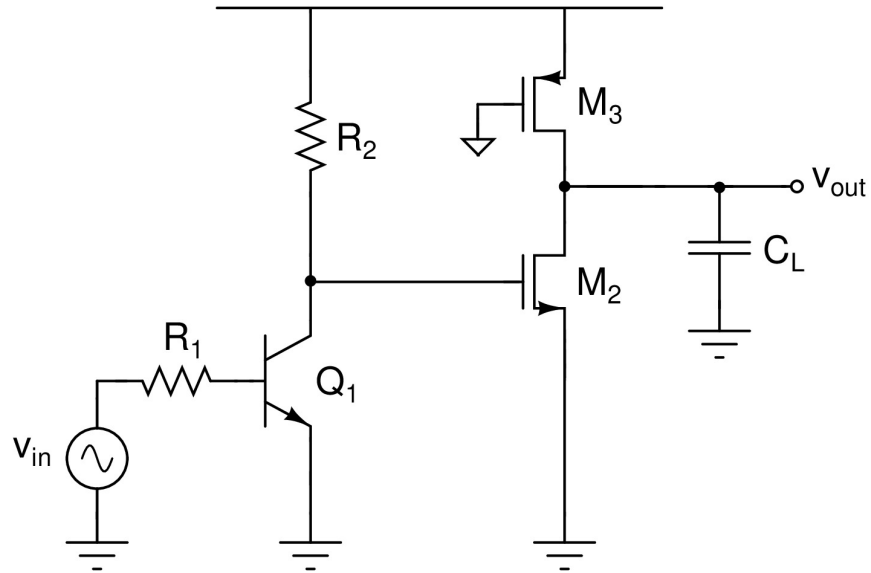
## Problem 2

Use the open-circuit time constant method to estimate the -3 dB frequency,  $\omega_{-3\text{dB}}$ , of this amplifier. Consider  $C_{gs}$ ,  $C_{gd}$ ,  $C_{\pi}$ ,  $C_{\mu}$ , and  $r_{ds}$ . Ignore  $r_o$ .


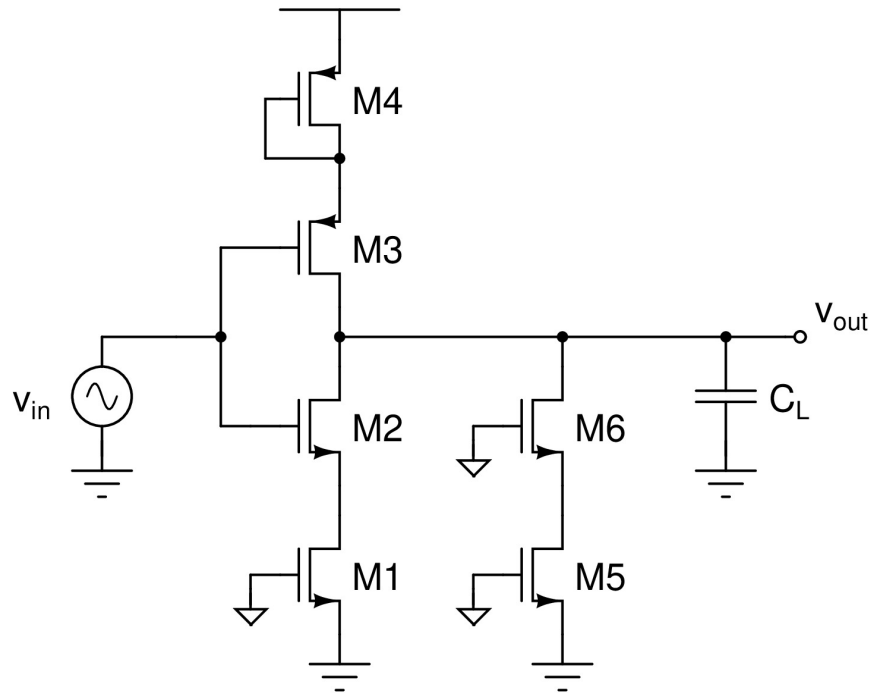
### Problem 3

Use the open-circuit time constant method to estimate the -3 dB frequency,  $\omega_{-3\text{dB}}$ , of this amplifier. Consider  $C_{gs}$ ,  $C_{gd}$ ,  $C_{\pi}$ ,  $C_{\mu}$ , and  $r_{ds}$ .



## CMOS Logic Circuits

For each part, design and draw the schematic of a CMOS logic gate that implements the Boolean expression. In each schematic, label the size of each transistor such that the worst case delays of the pull-up and pull-down networks are equivalent to those of a standard minimum-sized inverter with  $(W/L)_P/(W/L)_N = 2$ . Inverted inputs are not available.

(a)  $Z_1 = \overline{(A + B) \cdot C}$

(b)  $Z_2 = \overline{(A \cdot B \cdot C) + (D \cdot E)}$

(c)  $Z_3 = \overline{A} \cdot (\overline{B} + \overline{C} + \overline{D})$