

HKN ECE 120 Midterm 2 Worksheet

CMOS Logic

Problem 1


Draw the CMOS network for the following expressions:

- a. $Z = A'$
- b. $Z = (A \cdot B)'$
- c. $Z = (A + B)'$
- d. $Z = ((A + B) \cdot C)'$
- e. $Z = ((B \cdot C) + A)'$


Problem 2

Are these valid CMOS networks? If not, explain why.

a.

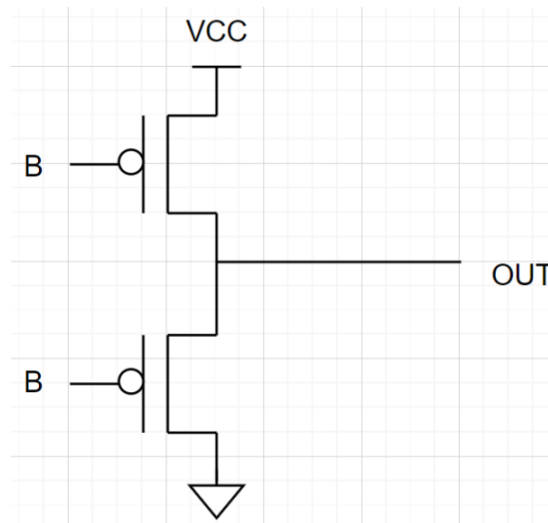

b.

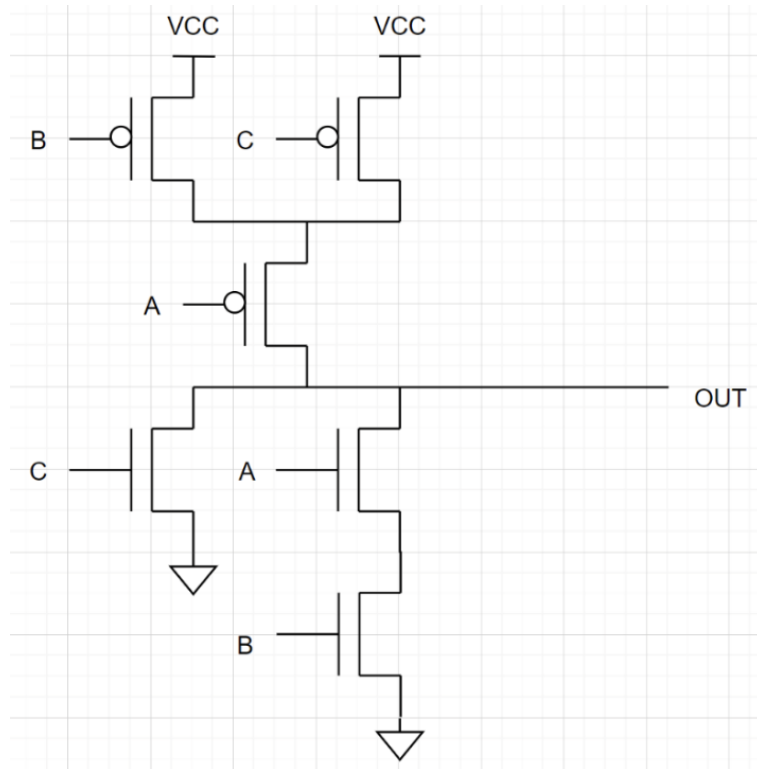

Boolean Expressions, Algebra, & Optimization

Problem 1


Simplify the following expressions:

- $F(A, B, C) = (A + B) \cdot (B' + C) \cdot (A + C)$
- $F(A, B, C) = A'BC + ABC + ABC' + AB'C$
- $F(A, B, C) = A' \cdot (A + B) + (A + B) \cdot (A + B')$

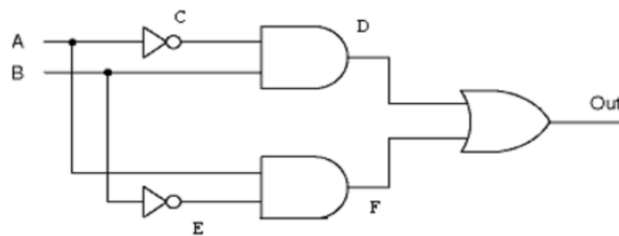
Problem 2

True or False:

- The delay for the following expression is 2.



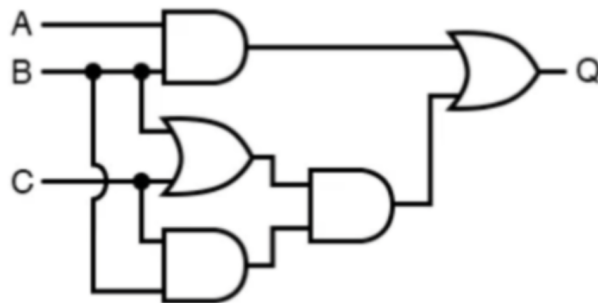- The area for the following expression is 7.



K-maps, SOP & POS Expressions

Problem 1

Use K-maps or simplification to find the minimal SOP and POS expressions for the following, then draw them in NAND/NOR form:

a.

B	C	D	Z
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

b.

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	X
0	1	1	1	X
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X


Adders, ALUs, and Bit-Slicing

Problem 1

Remember that the logical output for one slice of a full adder is:

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

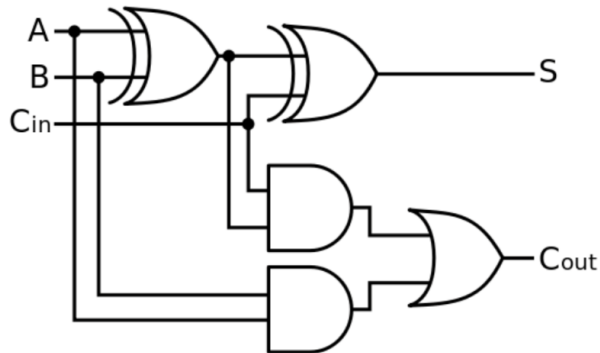- Find an expression for Cout and S using AND and OR gates.
- Consider the digital circuit:



Verify that it is equivalent to your expression.

Problem 2

Build each of these circuits using only adders, inverters, and fixed inputs (1 or 0). Do not account for overflows unless otherwise noted.

- For two 4-bit unsigned integers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$, calculate the 5-bit unsigned integer $S_4S_3S_2S_1S_0 = A + B$.
- For two 4-bit two's complement integers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$, calculate the 4-bit two's complement integer $S_3S_2S_1S_0$ where $S = A - B$.
- For three 3-bit two's complement integers $A_2A_1A_0$, $B_2B_1B_0$, $C_2C_1C_0$, calculate $S_2S_1S_0 = A + A - B - C$.

Problem 3

Assume an ALU that takes two 8-bit integers A and B as input and can calculate AB (AND),

- a. How many bits is the output S ?
- b. How many bits must the control signal be?
- c. Is the ALU logically complete? Assume you have 0 and 1 available.
- d. (Optional) Draw out the full circuit diagram for this ALU, using basic logic gates, MUXs, decoders, and full adders.

Problem 4

In 50 or fewer words, explain the advantages and disadvantages of bit-slicing over optimizing for many variables.

Multiplexers

Problem 1

Write down the truth table for a 2-to-1 multiplexer. Write an expression for the output, and implement the 2:1 MUX using AND gates, OR gates, and inverters.

Problem 2

Using the same process (you may not need the truth table), implement a 4:1 MUX using AND gates, OR gates, and inverters.

Problem 3

Implement a 4:1 MUX using three 2:1 MUXs.

Problem 4

Implement a 8:1 MUX using two 4:1 MUXs and a 2:1 MUX.

Decoders

Problem 1

In 20 words or less, what does a decoder do?

Problem 2

Implement a 2x4 decoder using AND gates, OR gates, and inverters.

Problem 3


Implement a 4x16 decoder using five 2x4 decoders. (Hint: you should use the ENABLE pin)

Latches & Flip-Flops


Problem 1

Find the stable states of the following latches:

a.

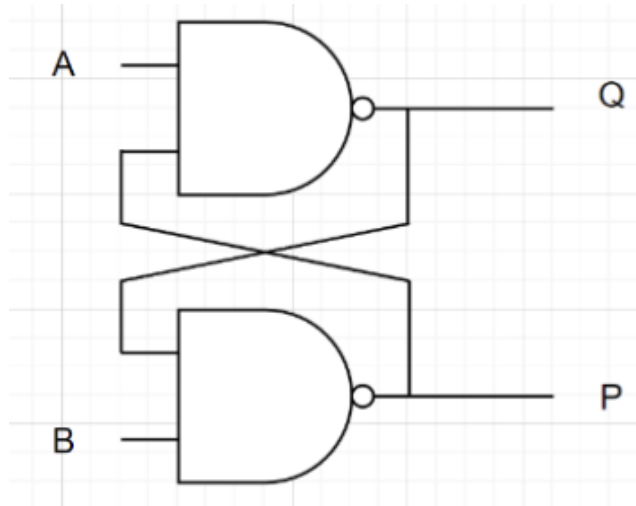


b.

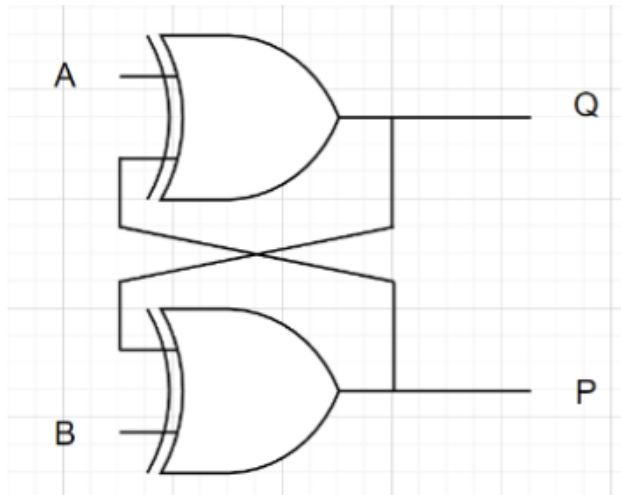

c. Which latch is more viable for data storage?

Problem 2

Explain the process of storing a bit of data in a D latch.

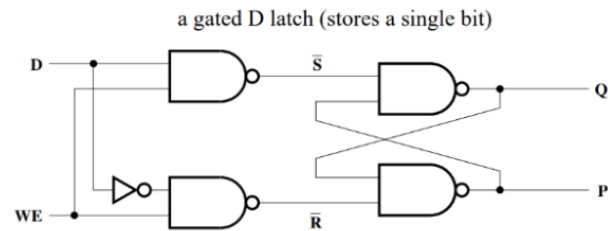

Problem 3

Explain the difference between a D latch and a D flip-flop.

Problem 4

Implement a 4-bit register using D flip-flops.

Problem 5


Implement a 4-bit shift register with MSB load using D flip-flops.

Problem 6

Implement a 4-bit circular shift register with 4-bit load using D flip-flops.

Problem 7

Consider this digital circuit below.

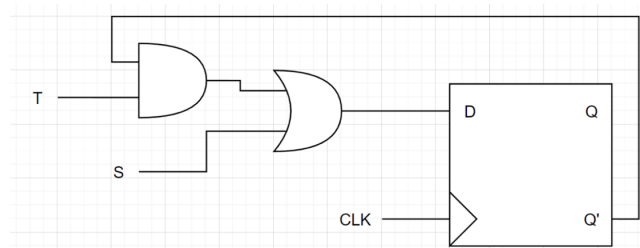

Assume at the start, $Q = 0$. Trace and fill out the table below. T and S signals are given in the table.

Clock Cycle #	Q	T	S	Q _{next}
0	0	1	0	
1		1	0	
2		0	0	
3		0	0	
4		0	1	

Problem 8

What are timing hazards? What are a few ways we can design around them? (Lumetta 2.6.3-2.6.5)

Serialized Design

Problem 1

Consider one bit-slice of a full adder.

- a. How many bits need to be passed between each bit slice? What are they?
- b. If we wanted to serialize this design and add 1 bit at a time, how many D flip-flops would we need to store these signals?
- c. Implement a serialized binary adder, adding 1 bit at a time.
- d. Assume we instead wanted to add 4 bits (1 hexadecimal) at a time. Would any signals be different?
- e. Implement a serialized binary adder, adding 4 bits at a time.

Problem 2

Consider a serialized circuit that takes a sequence of bits, 1 bit at a time, and outputs the same sequence of bits but is delayed by 2 bits and inverted. For example, assuming inputs and outputs are taken at the start of each clock cycle, if the input is 100101101100, then the output is XX0110100100.

- a. How many bits do we need to store between each clock cycle?
- b. Implement this circuit using D flip-flops.
- c. Can we also implement this circuit using a shift register?

Problem 3

In 50 words or less, what are the advantages and disadvantages of serialization over bit-slicing?